

CS251, Spring 2022

Assignment 1: Question 3

Q3a) Give the unreduced sum of products expression for F:

$$F = X\bar{Y}Z + XY\bar{Z} + XYZ$$

Q3b) Draw a circuit that implements F:

